

**ĐẠI HỌC QUỐC GIA THÀNH PHỐ HỒ CHÍ MINH**  
**TRƯỜNG ĐẠI HỌC BÁCH KHOA**  
**KHOA ĐIỆN – ĐIỆN TỬ**



**BÁO CÁO THÍ NGHIỆM THIẾT KẾ VI MẠCH**  
**MINI PROJECT 3**

LỚP: L01 ---- NHÓM: 01

STT	Sinh viên thực hiện	Mã số sinh viên
1	Lê Quốc Thái	2114764
2	Nguyễn Khánh Huy	2113510
3	Nguyễn Thành Phát	2114378
4	Nguyễn Ngọc Kiều Duyên	2113053
5	Huỳnh Thịnh Phát	2114369

*Thành phố Hồ Chí Minh – 2024*

**DANH SÁCH THÀNH VIÊN**

<b>STT</b>	<b>Sinh viên thực hiện</b>	<b>Mã số sinh viên</b>	<b>Đóng góp</b>
1	Lê Quốc Thái	2114764	100%
2	Nguyễn Khánh Huy	2113510	100%
3	Nguyễn Thành Phát	2114378	100%
4	Nguyễn Ngọc Kiều Duyên	2113053	100%
5	Huỳnh Thịnh Phát	2114369	100%

## MỤC LỤC

DANH SÁCH THÀNH VIÊN.....	1
MỤC LỤC .....	2
DANH SÁCH HÌNH ẢNH.....	3
DANH SÁCH BẢNG .....	4
MINI PROJECT 3: DESIGN AND SYNTHESIZE ALU.....	5
Requirements .....	5
Block diagrams of the design .....	5
Port definations.....	6
Below table is the detailed function of the ALU design .....	6
Flow chart of the design .....	7
Timing report with frequency at 1GHz .....	7
Total area .....	7
Gates usage .....	8
Verification plan .....	9
Simulate the design and fill in the verification plan.....	9
RTL.....	10
Netlist.....	11

**DANH SÁCH HÌNH ẢNH**

Hình 1: ALU Diagram .....	5
Hình 2: ALU flow chart.....	7
Hình 3: Timing report .....	7
Hình 4: Total area .....	7
Hình 5: Gate usage.....	8
Hình 6: Waveform ALU .....	9
Hình 7: RTL of ALU .....	10
Hình 8: Netlist of ALU .....	11

**DANH SÁCH BẢNG**


Bảng 1: Port definitions.....	6
Bảng 2: Detail function of ALU .....	6
Bảng 3: Verification plan.....	9
Bảng 4: Verification plan after test.....	10

**MINI PROJECT 3: DESIGN AND SYNTHESIZE ALU****Requirements**

- Design a basic ALU, sampled at positive edge of clock, asynchronous reset, when reset is asserted, result is 0.

The ALU can perform these operations:

- Addition, Subtraction
- Bitwise AND, OR, XOR, NOT
- Logical shift left, logical shift right.

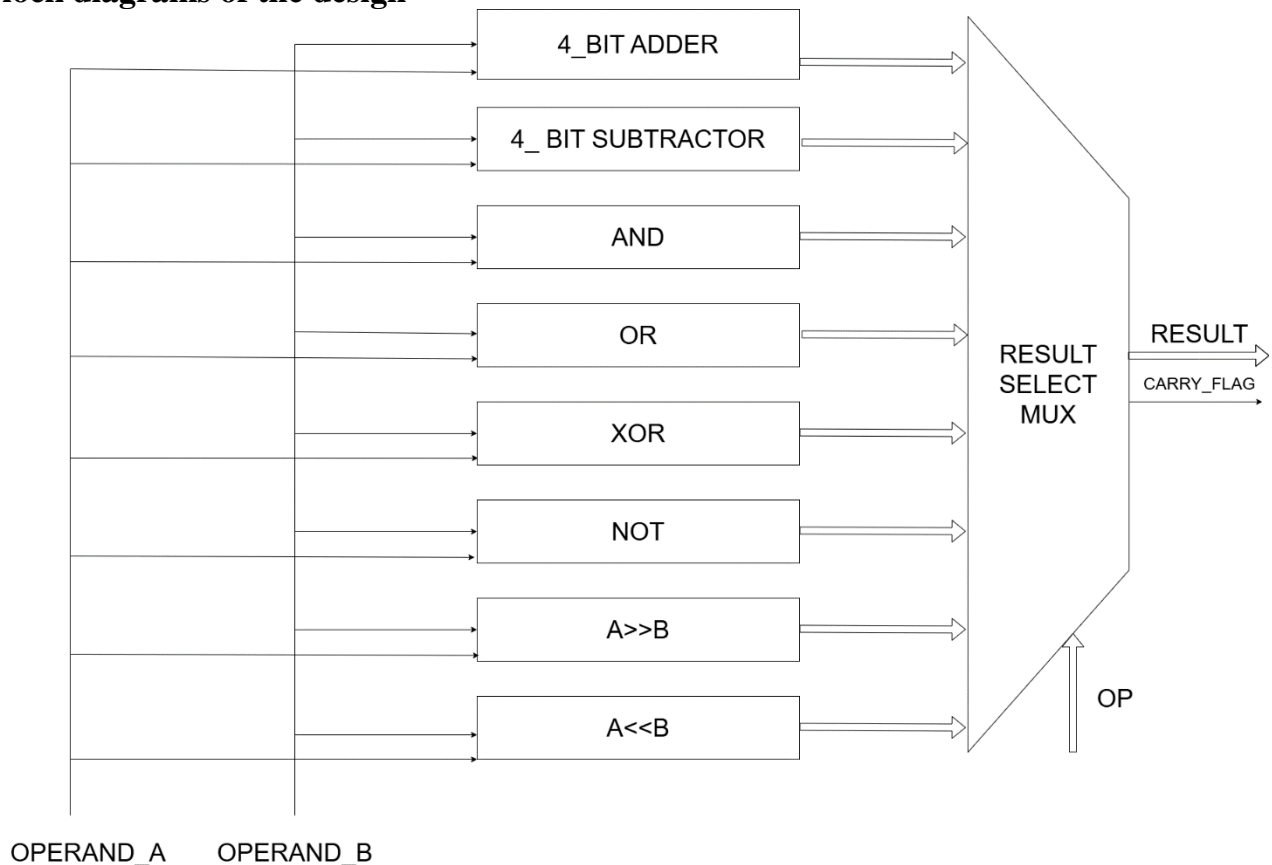**Block diagrams of the design**

Hình 1: ALU Diagram

**Port definations**

Signal	Width	Type	Description
clk_i	1	input	Positive clock signal
rst_ni	1	input	Negative edge reset. If rst_ni = 0, result and carry will be set to 0. Else, the design will work normally base on the input arguments
a_i	4	input	First argument
b_i	4	input	Second argument
op_i	3	input	Select the operation
result_o	4	output	Result of ALU
carry_o	1	output	Carry flag


Bảng 1: Port definations

**Below table is the detailed function of the ALU design**

Operation (op_i)	Description
3'b000	{ carry_o,result_o } = a_i + b_i
3'b001	{ carry_o,result_o } = a_i - b_i
3'b010	carry_o = 0; result_o = and (a_i,b_i)
3'b011	carry_o = 0; result_o = or (a_i,b_i)
3'b100	carry_o = 0; result_o = xor (a_i,b_i)
3'b101	carry_o = 0; result_o = not (a_i)
3'b110	carry_o = 0; result_o = a_i >> b_i
3'b111	carry_o = 0; result_o = a_i << b_i

Bảng 2: Detail function of ALU

## Flow chart of the design

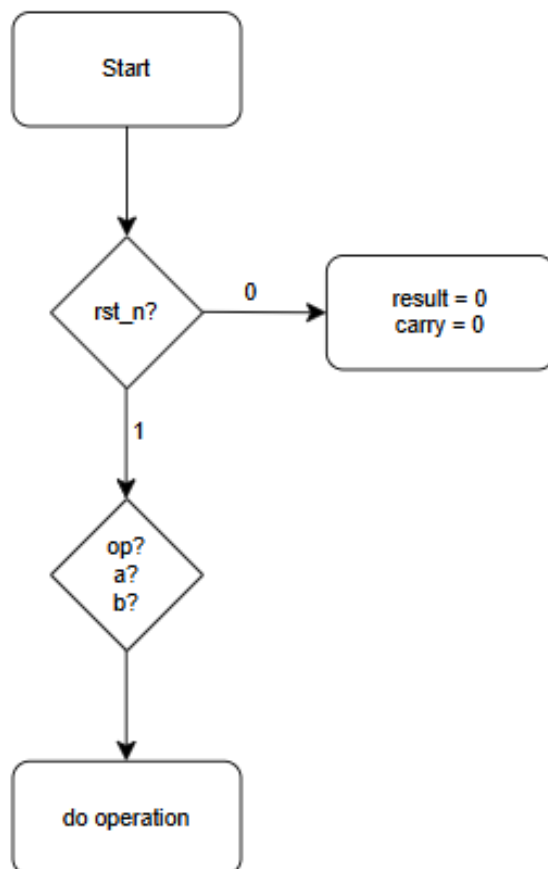

Hình 2: ALU flow chart

## Timing report with frequency at 1GHz

```

[admin@centos7 synthesis]$ make report
with Frequency at:
set FREQ_GHz 1.0
Path 1: MET (0 ps) Setup Check with Pin result_add_reg[2]/CLK->D
Path 2: MET (0 ps) Setup Check with Pin result_reg[0]/CLK->D
Path 3: MET (0 ps) Setup Check with Pin result_reg[2]/CLK->D
Path 4: MET (0 ps) Setup Check with Pin result_reg[3]/CLK->D
Path 5: MET (1 ps) Setup Check with Pin result_add_reg[3]/CLK->D
Path 6: MET (1 ps) Setup Check with Pin result_subtractor_reg[3]/CLK->D
Path 7: MET (2 ps) Setup Check with Pin a_shift_right_reg[2]/CLK->D
Path 8: MET (3 ps) Setup Check with Pin result_reg[1]/CLK->D
Path 9: MET (4 ps) Setup Check with Pin a_shift_left_reg[2]/CLK->D
Path 10: MET (5 ps) Setup Check with Pin a_shift_right_reg[0]/CLK->D
  
```

Hình 3: Timing report

## Total area

Instance	Cells	Cell Area	Net Area	Total Area
alu	229	1866	1208	3074

Hình 4: Total area



## Gates usage

 
sky130_fd_sc_hd_inv_4	4	25.024	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_inv_6	4	35.034	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_inv_8	2	22.522	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nand2_1	43	161.405	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nand2_2	15	93.840	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nand2_4	15	168.912	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nand2_8	2	40.038	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nand2b_1	4	25.024	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nand3_1	17	85.082	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nand3_2	4	40.038	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nand3b_1	6	45.043	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nand4_1	9	56.304	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nand4b_1	1	8.758	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nor2_1	10	37.536	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nor2_2	10	62.560	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nor2_4	3	33.782	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nor2_8	1	20.019	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nor2b_1	2	12.512	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_o211ai_1	1	7.507	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_o21a_1	1	7.507	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_o21ai_1	9	45.043	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_o21ai_2	3	26.275	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_o21ai_4	1	16.266	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_o22ai_1	1	6.256	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_o2bb2ai_1	1	8.758	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_o2bb2ai_4	1	27.526	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_xnor2_1	1	8.758	sky130_fd_sc_hd_tt_025C_1v80
-----			
total	229	1865.539	
Type	Instances	Area	Area %
-----			
sequential	22	515.494	27.6
inverter	39	247.738	13.3
logic	168	1102.307	59.1
-----			
total	229	1865.539	100.0

Hình 5: Gate usage

**Verification plan**

Section	Item	Description	Testcase name	Owner	Status
1	Reset	When rst_ni asserted, the output is 0, when it de-asserts, the design will work normally	rst_test	N1	PASS
2	Operation test	When op_i is set 3'b000 to 3'b111. At the same 2 arguments. Check the result_o and carry_o. The argument will be a_i = 4'b1011 and b_i = 4'b0100	operation_test	N1	RUNNING
3	Carry test	The argument will be a_i = 4'b1111 and b_i = 4'b1111. The op_i = 3'b000 and 3'b001. Check the result_o and carry_o	cary_test	N1	RUNNING

Bảng 3: Verification plan

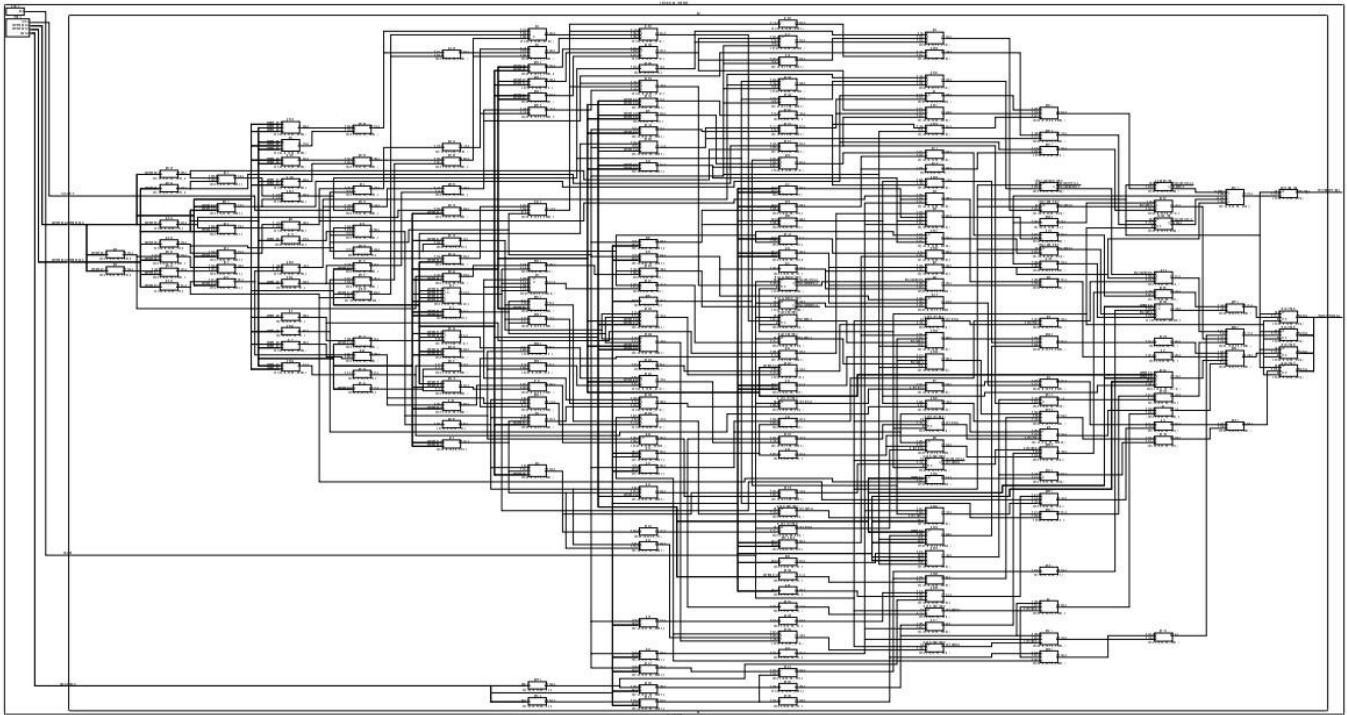
**Simulate the design and fill in the verification plan**

Hình 6: Waveform ALU

Section	Item	Description	Testcase name	Owner	Status
1	Reset	When rst_ni asserted, the output is 0, when it de-asserts, the design will work normally	rst_test	N1	PASS
2	Operation test	When op_i is set 3'b000 to 3'b111. At the same 2 arguments. Check the result_o and carry_o. The argument will be a_i = 4'b1011 and b_i = 4'b0100	operation_test	N1	PASS


3	Carry test	The argument will be $a_i = 4'b1111$ and $b_i = 4'b1111$ . The $op_i = 3'b000$ and $3'b001$ . Check the $result_o$ and $carry_o$	cary_test	N1	PASS
---	------------	--	-----------	----	------

Bảng 4: Verification plan after test

**RTL**

Hình 7: RTL of ALU

## Netlist

 

Hình 8: Netlist of ALU