

**ĐẠI HỌC QUỐC GIA THÀNH PHỐ HỒ CHÍ MINH**  
**TRƯỜNG ĐẠI HỌC BÁCH KHOA**  
**KHOA ĐIỆN – ĐIỆN TỬ**



**BÁO CÁO THÍ NGHIỆM THIẾT KẾ VI MẠCH**  
**LAB 3: LOGIC SYNTHESIS AND VLSI**  
**FRONT-END FLOW**

LỚP: L01 ---- NHÓM: 01

STT	Sinh viên thực hiện	Mã số sinh viên
1	Lê Quốc Thái	2114764
2	Nguyễn Khánh Huy	2113510
3	Nguyễn Thành Phát	2114378
4	Nguyễn Ngọc Kiều Duyên	2113053
5	Huỳnh Thịnh Phát	2114369

*Thành phố Hồ Chí Minh – 2024*

## DANH SÁCH THÀNH VIÊN

STT	Sinh viên thực hiện	Mã số sinh viên	Đóng góp
1	Lê Quốc Thái	2114764	100%
2	Nguyễn Khánh Huy	2113510	100%
3	Nguyễn Thành Phát	2114378	100%
4	Nguyễn Ngọc Kiều Duyên	2113053	100%
5	Huỳnh Thịnh Phát	2114369	100%

## MỤC LỤC

DANH SÁCH THÀNH VIÊN.....	1
MỤC LỤC .....	2
DANH SÁCH HÌNH ẢNH.....	3
DANH SÁCH BẢNG .....	4
LAB 3: DESIGN AND SYNTHESIZE “4-BIT COUNTER” .....	5
Requirements .....	5
Block diagrams of the design .....	5
Port definitions:.....	5
Flow chart of the design .....	6
Timing report with frequency at 1GHz .....	6
Total area .....	6
Gates usage .....	7
Verification plan .....	7
Simulate the design and fill in the verification plan.....	8
RTL.....	9
Netlist.....	9

**DANH SÁCH HÌNH ẢNH**


Hình 1: Diagram 4-bit counter.....	5
Hình 2: Flow chart 4-bit counter.....	6
Hình 3: Timing report .....	6
Hình 4: Total area .....	6
Hình 5: Gate usage.....	7
Hình 6: Waveform 4-bit counter.....	8
Hình 7: RTL 4-bit counter .....	9
Hình 8: Netlist 4-bit counter .....	9

**DANH SÁCH BẢNG**

Bảng 1: Port definations.....	5
Bảng 2: Verification plan.....	7
Bảng 3: Verification plan after test.....	8

**LAB 3: DESIGN AND SYNTHESIZE “4-BIT COUNTER”****Requirements**

Design a 4-bit counter, sampled at the positive edge of clock signal, with an asynchronously active-low reset. When rst\_ni asserted, the output is 0. It can either count up or count down based on the user's needs.

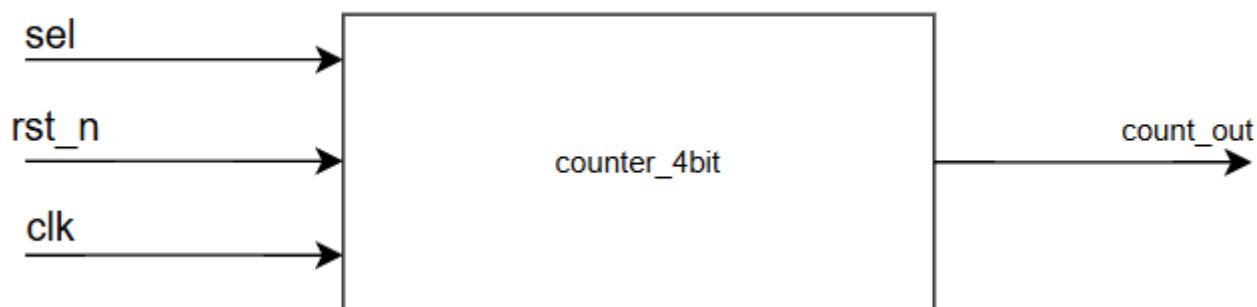 
**Block diagrams of the design**

Hình 1: 4-bit counter Diagram

**Port definations:**

Signal	Width	Type	Description
clk_i	1	input	Positive clock signal
rst_ni	1	input	Negative edge reset. If rst_ni = 0, output will be set to 0. Else, it will start the normal operation
sel_i	1	input	Mode selection signal. If sel_i = 1, the design will start counting up else, it will staer counting down from the current output value.
counter_o	4	output	Result of the design

Bảng 1: Port definations

**Flow chart of the design**

Hình 2: Flow chart 4-bit counter

**Timing report with frequency at 1GHz**

```

set FREQ_GHz 1.0
Path 1: MET (0 ps) Setup Check with Pin out_reg[3]/CLK->D
Path 2: MET (80 ps) Late External Delay Assertion at pin out[2]
Path 3: MET (82 ps) Setup Check with Pin out_reg[2]/CLK->D
Path 4: MET (85 ps) Late External Delay Assertion at pin out[0]
Path 5: MET (99 ps) Late External Delay Assertion at pin out[1]
Path 6: MET (112 ps) Late External Delay Assertion at pin out[3]
Path 7: MET (157 ps) Setup Check with Pin out_reg[1]/CLK->D
Path 8: MET (434 ps) Setup Check with Pin out_reg[0]/CLK->D
  
```

Hình 3: Timing report

**Total area**

Instance	Cells	Cell Area	Net Area	Total Area
counter	19	205	98	303

Hình 4: Total area

**Gates usage**

Gate	Instances	Area	Library
sky130_fd_sc_hd_clkinv_2	1	5.005	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_dfrtp_1	3	75.072	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_dfrtp_2	1	26.275	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_inv_2	2	7.507	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nand2_1	3	11.261	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nand2_2	1	6.256	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nand3b_1	1	7.507	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_nor2_2	1	6.256	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_o2bb2ai_1	1	8.758	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_xnor2_1	2	17.517	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_xor2_1	2	17.517	sky130_fd_sc_hd_tt_025C_1v80
sky130_fd_sc_hd_xor2_2	1	16.266	sky130_fd_sc_hd_tt_025C_1v80
total	19	205.197	

Type	Instances	Area	Area %
sequential	4	101.347	49.4
inverter	3	12.512	6.1
logic	12	91.338	44.5
total	19	205.197	100.0

Hình 5: Gate usage


**Verification plan**

Section	Item	Description	Testcase name	Owner	Status
1	Reset	When rst_n is asserted, the output is 0, when rst_n is de-asserts, the output start to count up each positive edge of clock	cnt_rst_test	N1	PASS
2	Max count	When output is 4'b1111 and the counter is counting up, the next positive edge clock, output will be 4'b0000	cnt_max_count_test	N1	RUNNING
3	Min count	When output is 4'0000 and the counter is counting down, the next positive edge clock, output will be 4'b1111	cnt_min_count_test	N1	RUNNING
4	Count up Count down	When rst_n is de-asserts, the output start to count up is 4'b1010 then rst_n is asserts, when rst_n asserts counting down from 4'b1111	cnt_up_down_test	N1	RUNNING

Bảng 2: Verification plan



## Simulate the design and fill in the verification plan

 

Hình 6: Waveform 4-bit counter

From #0 to #110, sel = 0, so 'out' decreases by 1 every 10 ps.


From #110 to #320, sel = 1, so 'out' increases by 1 every 10 ps.

At #210, rst\_n = 0, so 'out' is set to 0.

Section	Item	Description	Testcase name	Owner	Status
1	Reset	When rst_n is asserted, the output is 0, when rst_n is de-asserts, the output start to count up each positive edge of clock	cnt_rst_test	N1	PASS
2	Max count	When output is 4'b1111 and the counter is counting up, the next positive edge clock, output will be 4'b0000	cnt_max_count_test	N1	PASS
3	Min count	When output is 4'0000 and the counter is counting down, the next positive edge clock, output will be 4'b1111	cnt_min_count_test	N1	PASS
4	Count up Count down	When rst_n is de-asserts, the output start to count up is 4'b1010 then rst_n is asserts, when rst_n asserts counting down from 4'b1111	cnt_up_down_test	N1	PASS


Bảng 3: Verification plan after test

## RTL

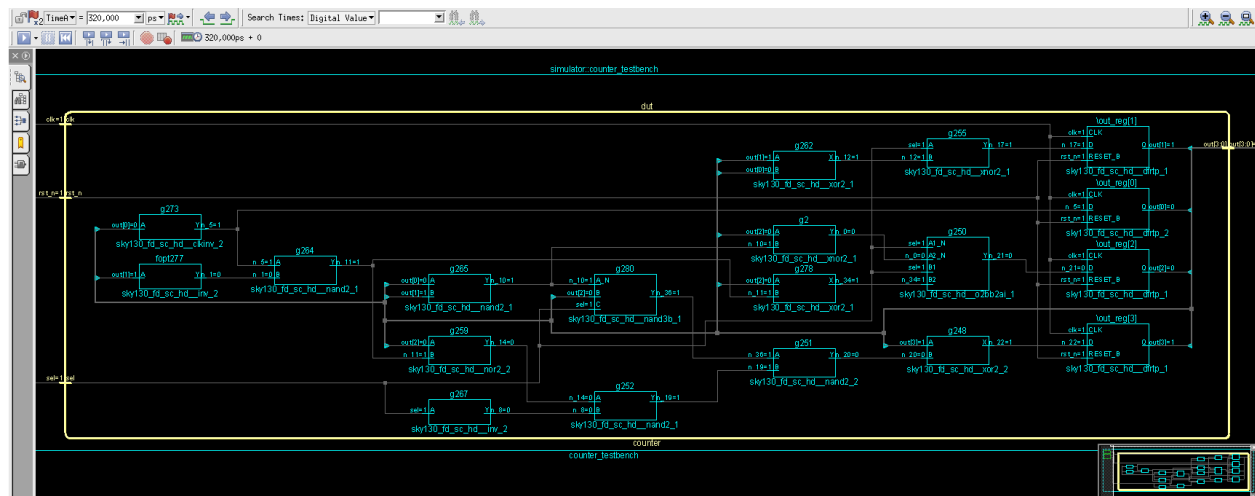

Hình 7: RTL 4-bit counter

## Netlist

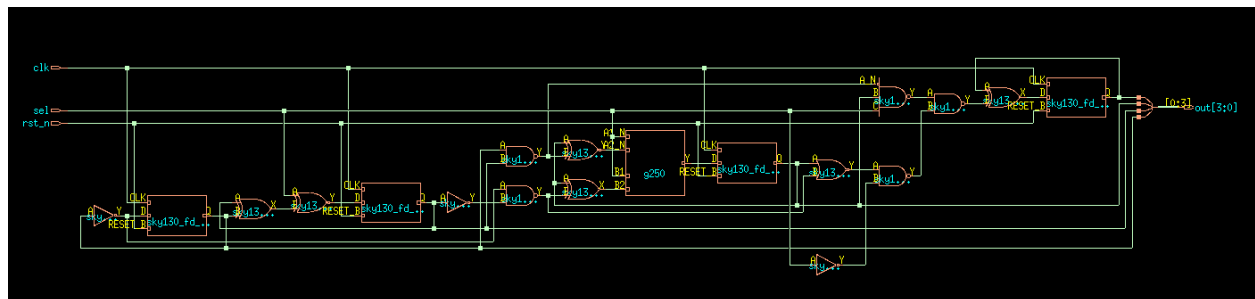

Hình 8: Netlist 4-bit counter