

ĐẠI HỌC QUỐC GIA THÀNH PHỐ HỒ CHÍ MINH
TRƯỜNG ĐẠI HỌC BÁCH KHOA
KHOA ĐIỆN – ĐIỆN TỬ



BÁO CÁO THÍ NGHIỆM THIẾT KẾ VI MẠCH
MINI PROJECT 1
LỚP: L01 ---- NHÓM: 01

STT	Sinh viên thực hiện	Mã số sinh viên
1	Lê Quốc Thái	2114764
2	Nguyễn Khánh Huy	2113510
3	Nguyễn Thành Phát	2114378
4	Nguyễn Ngọc Kiều Duyên	2113053
5	Huỳnh Thịnh Phát	2114369

Thành phố Hồ Chí Minh – 2024

DANH SÁCH THÀNH VIÊN

STT	Sinh viên thực hiện	Mã số sinh viên	Đóng góp
1	Lê Quốc Thái	2114764	100%
2	Nguyễn Khánh Huy	2113510	100%
3	Nguyễn Thành Phát	2114378	100%
4	Nguyễn Ngọc Kiều Duyên	2113053	100%
5	Huỳnh Thịnh Phát	2114369	100%

MỤC LỤC

DANH SÁCH THÀNH VIÊN	2
MỤC LỤC	3
EXPERIMENT 3	4
I. XOR.....	4
1. Truth table, schematic, symbol.....	4
2. Layout.....	5
II. FULL ADDER 1-BIT	7
1. Truth table, schematic, symbol.....	7
2. DC analysis, transient simulation	8
3. Layout.....	10

EXPERIMENT 3

Objective: Design a combinational circuit - a 1-bit Full Adder.


I. XOR

1. Truth table, schematic, symbol


- XOR truth table:

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

- XOR schematic:

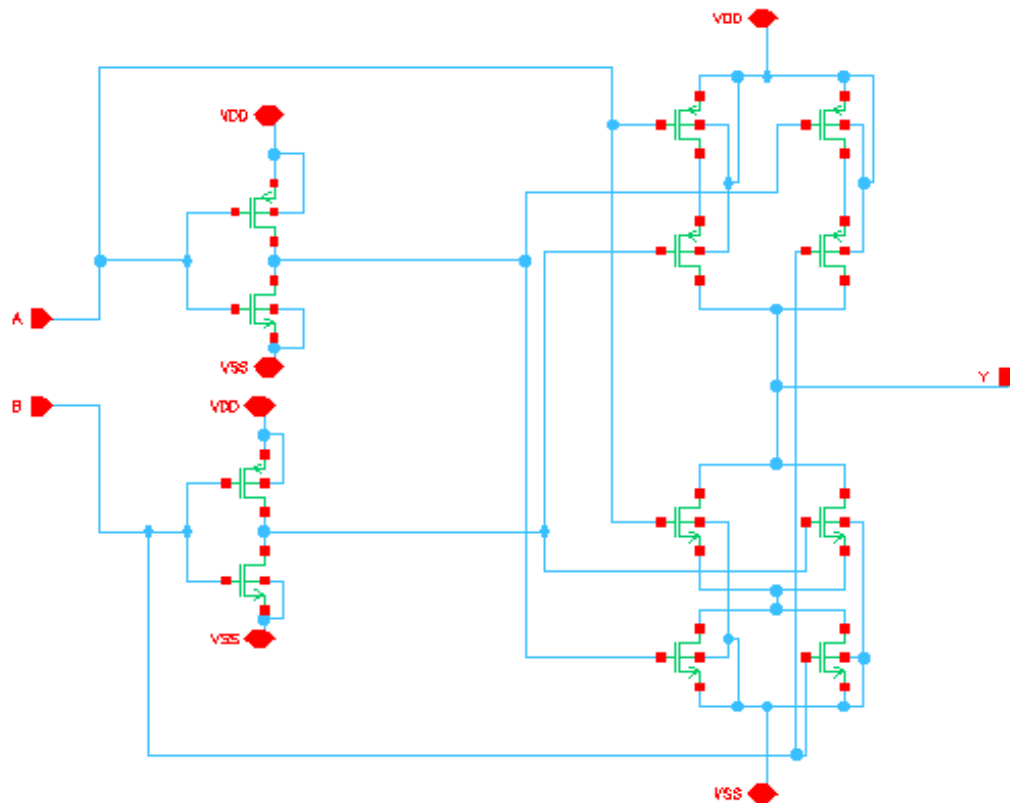


- XOR symbol:

 


2. Layout


- XOR layout:

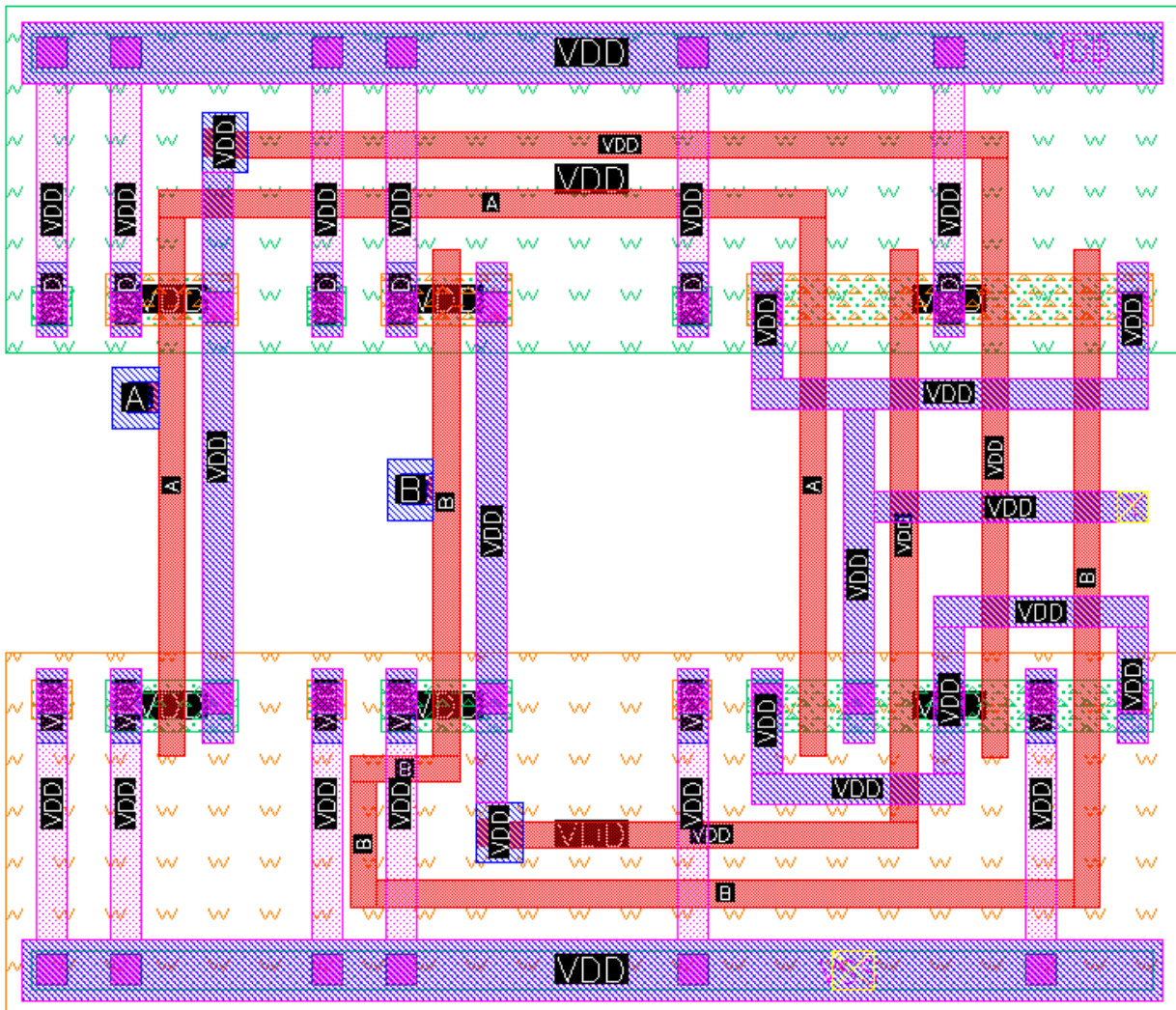

- XOR DRC:

 

- XOR LVS:

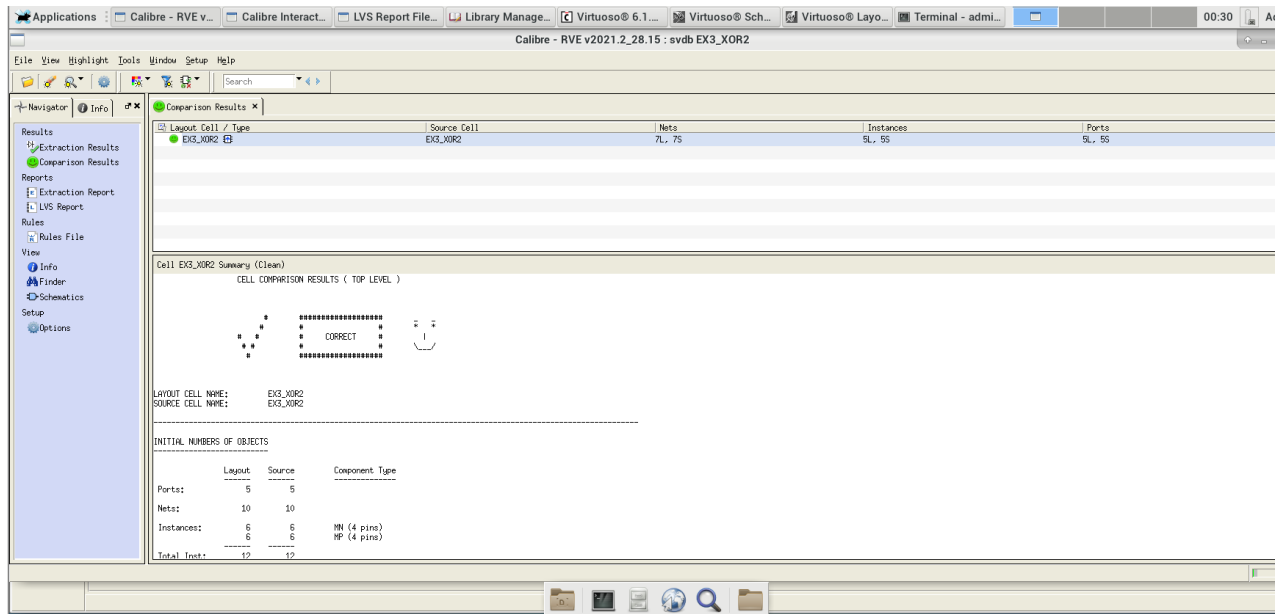


II. FULL ADDER 1-BIT

1. Truth table, schematic, symbol


- Full adder 1-bit truth table:

Input			Ouput	
A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- Full adder 1-bit schematic:

 


- Full adder 1-bit Symbol:

 


2. DC analysis, transient simulation


- Full adder 1-bit DC analysis:

 


- Transient simulation

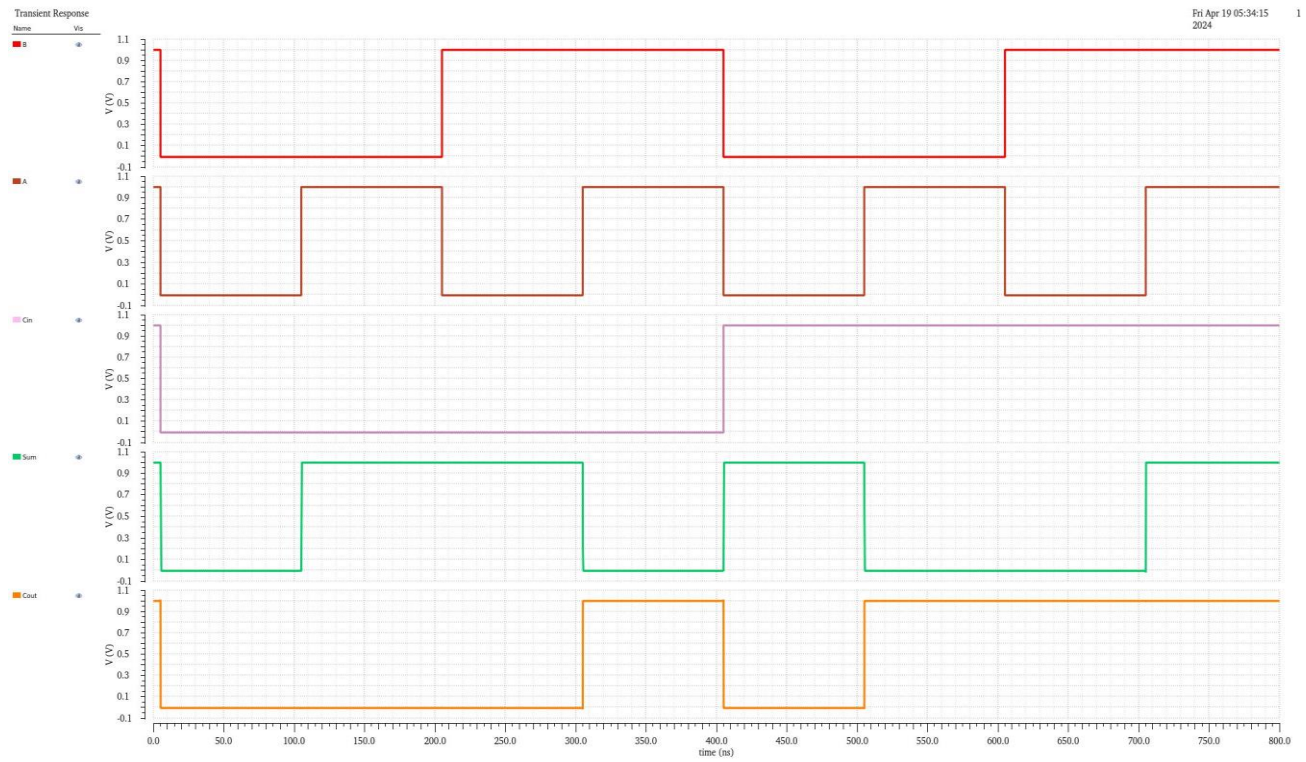

- Full adder 1-bit layout

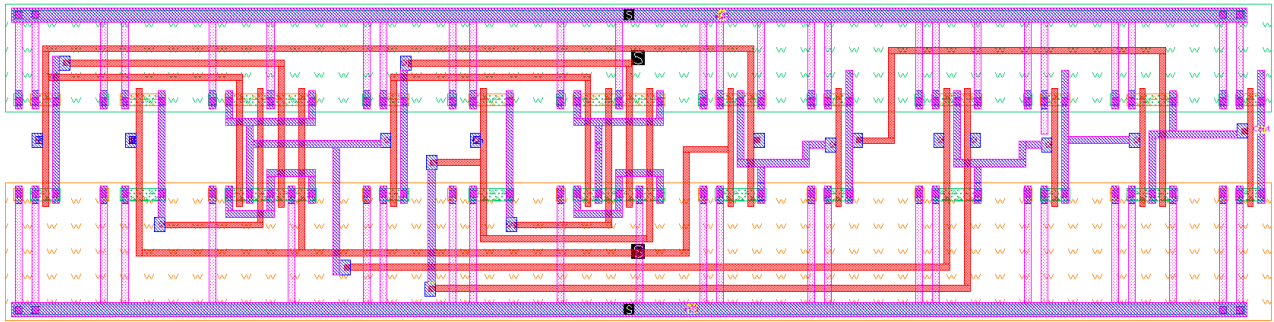

- Full adder 1-bit check DRC

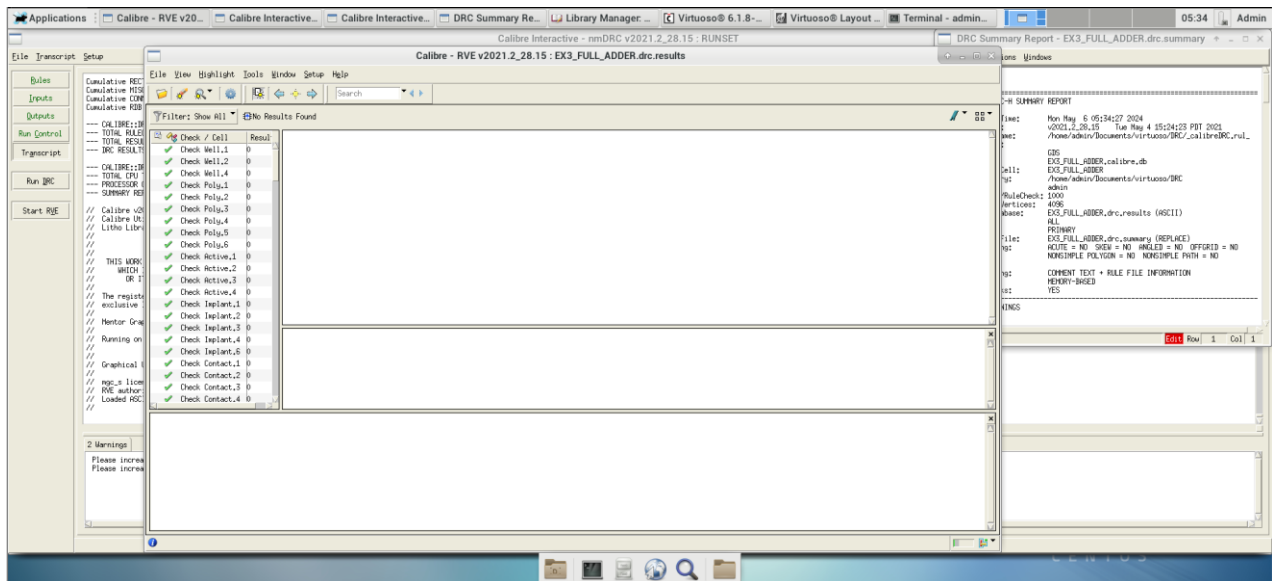

- Full adder 1-bit check LVS

